

## LAB ASSESSMENT -1

NAME: Rahul Mahesh Awari

REGISTER NUMBER: 18BEC2014

SUBJECT : VLSI SYSTEM DESIGN (ECE3002-ELA)

SLOT : L43 + L44



FACULTY : PROF. JAGANNADHA NAIDU K

# NMOS

**AIM:-** To calculate and plot following for NMOS and PMOS.


- 1) Plot  $I_{ds}$  vs  $V_{ds}$  with variable  $V_{gs}$
- 2) Calculate Channel length modulation.
- 3) For Plot of  $I_{ds}$  vs  $V_{gs}$  calculate  $I(\text{reference})$ , reference current
- 4) Plot  $I_{ds}$  vs  $V_{gs}$  for variable  $V_{sb}$

**Schematic:-**

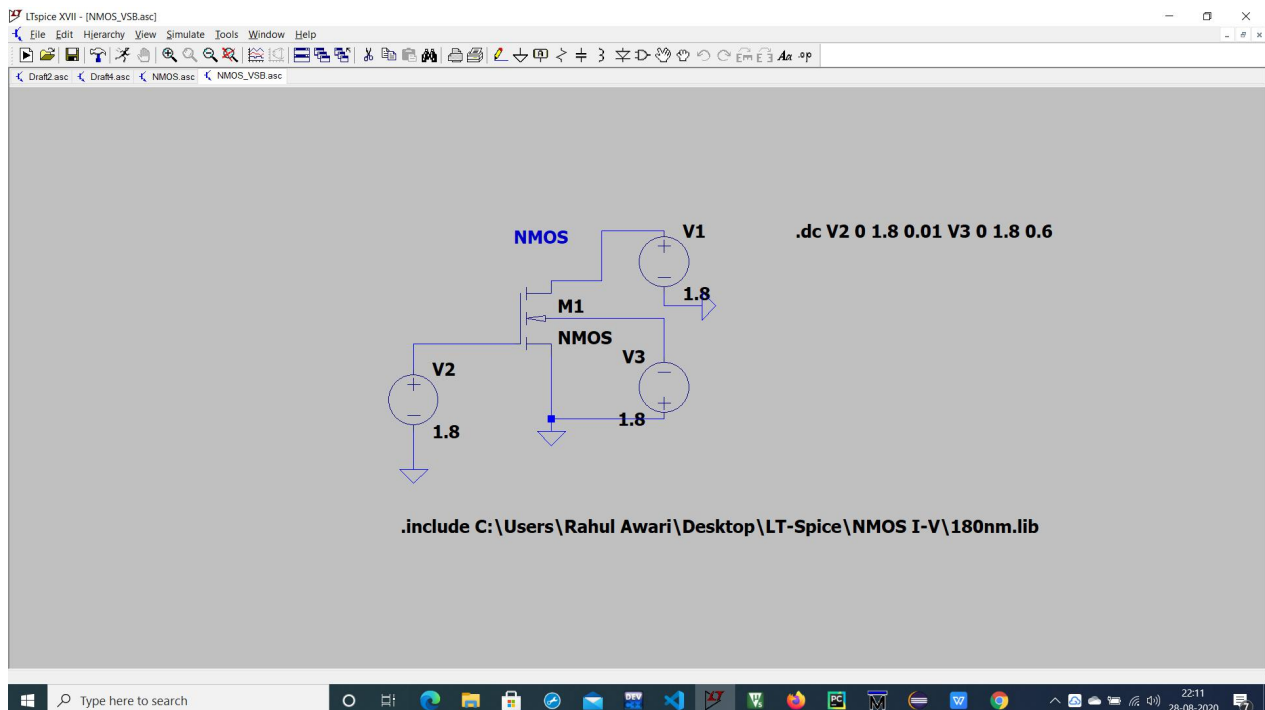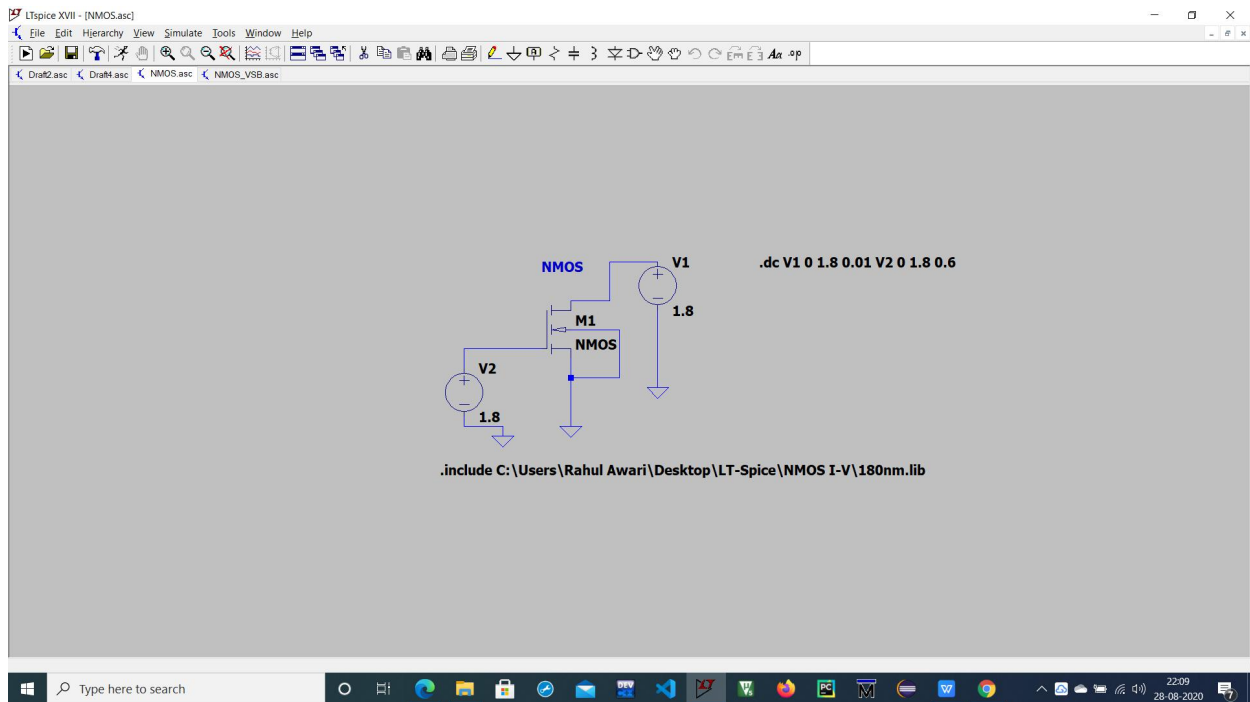


## GRAPHS:-


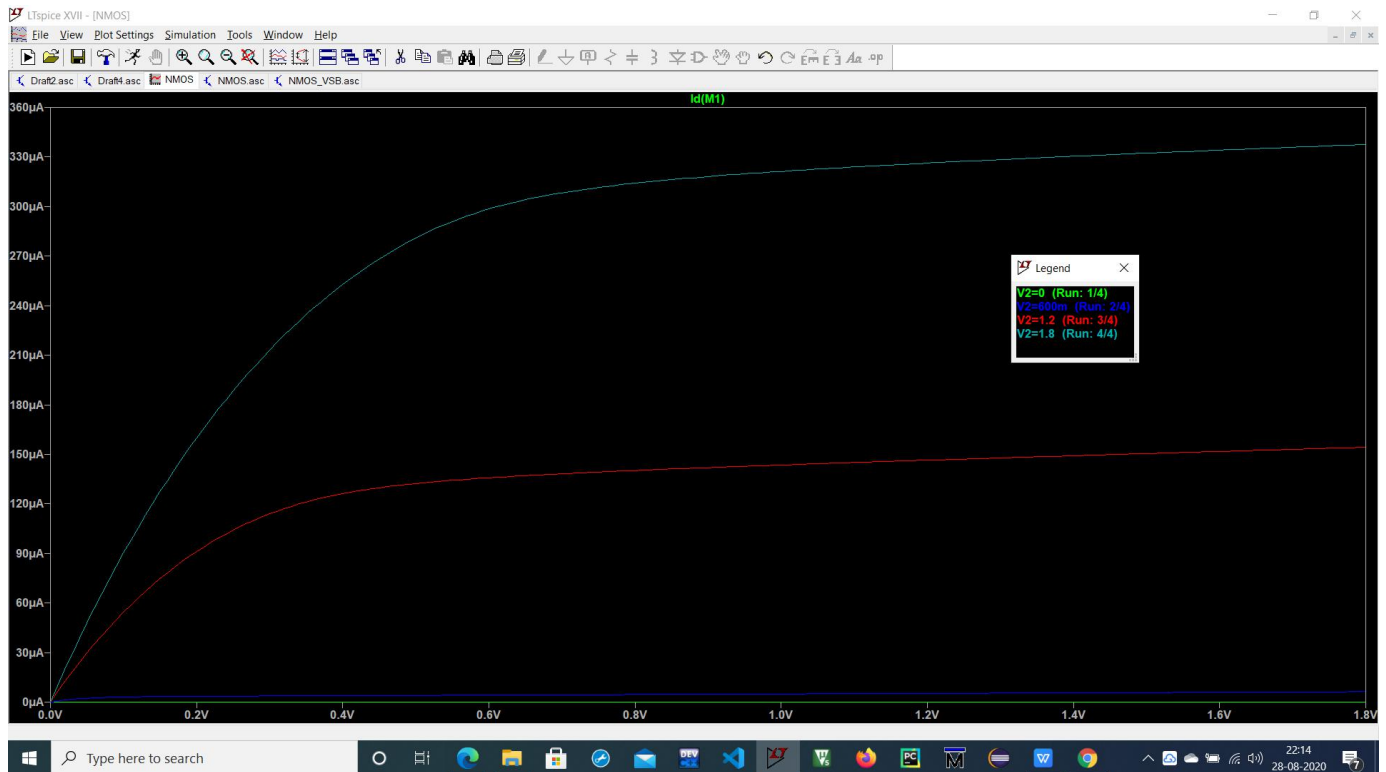
### 1) Plot $I_d$ vs $V_{ds}$ (with $V_{gs}$ (0→1.8V) with interval of 0.6V)


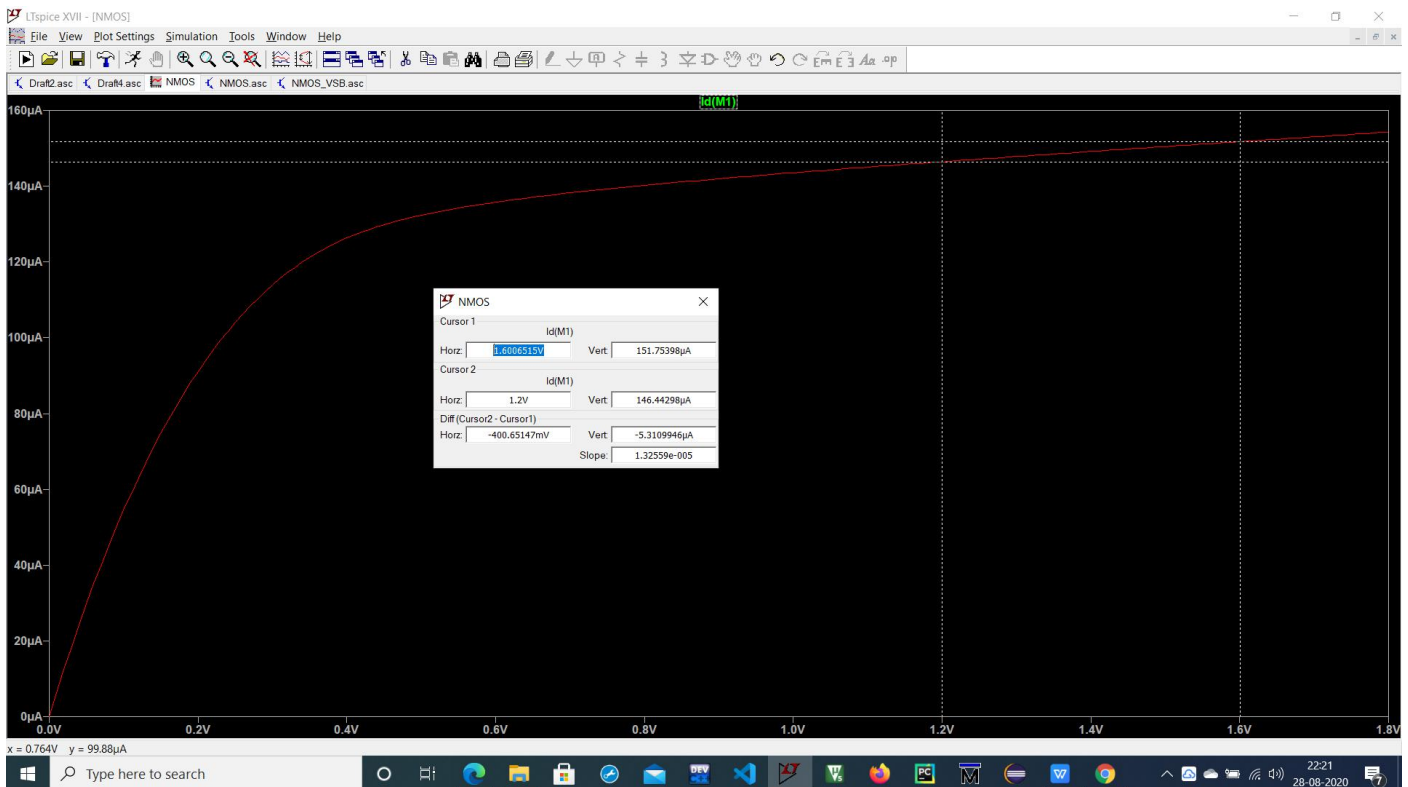
### 2) To Plot and find $I_{ds1}$ and $I_{ds2}$ at $V_{ds1}=1.6V$ and $V_{ds2}=1.2V$ for $V_{gs}=1.2V$



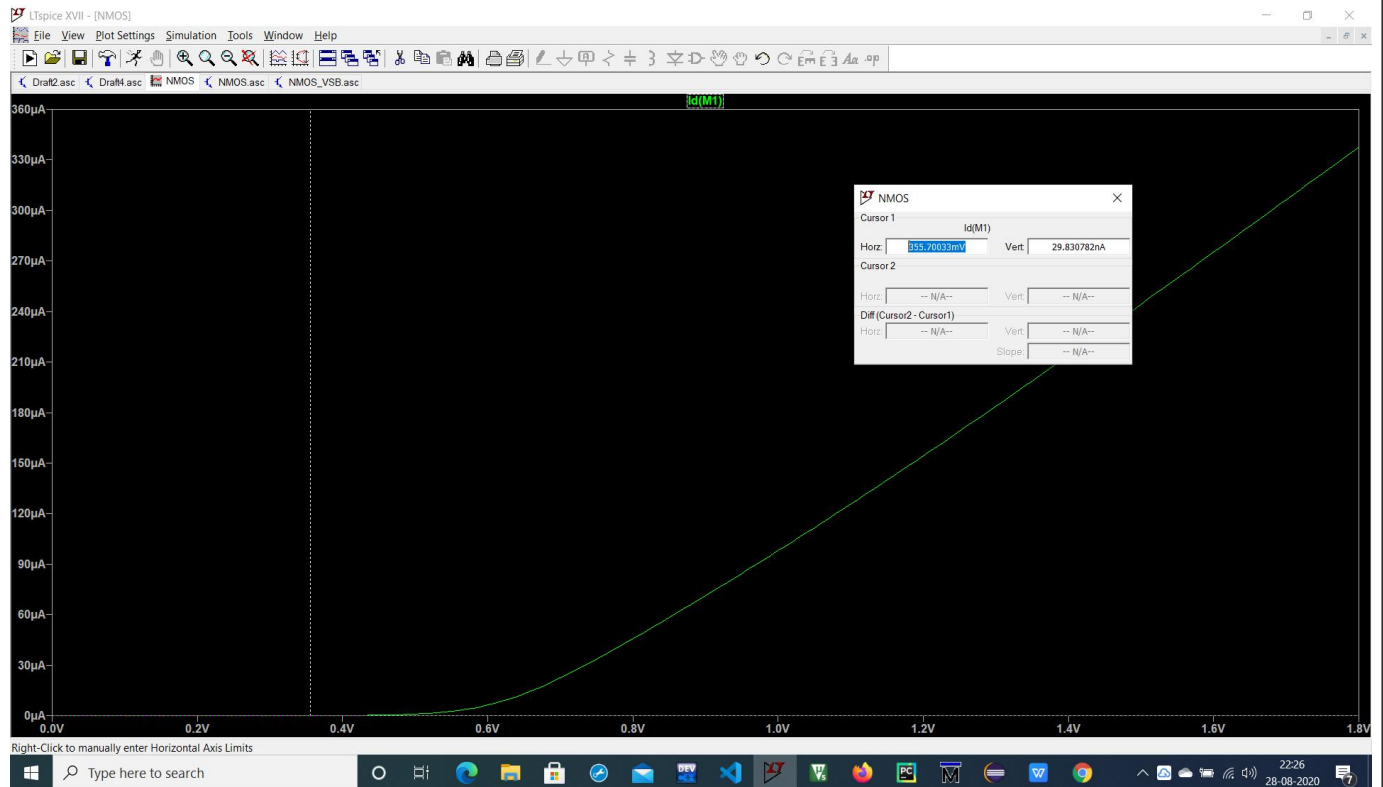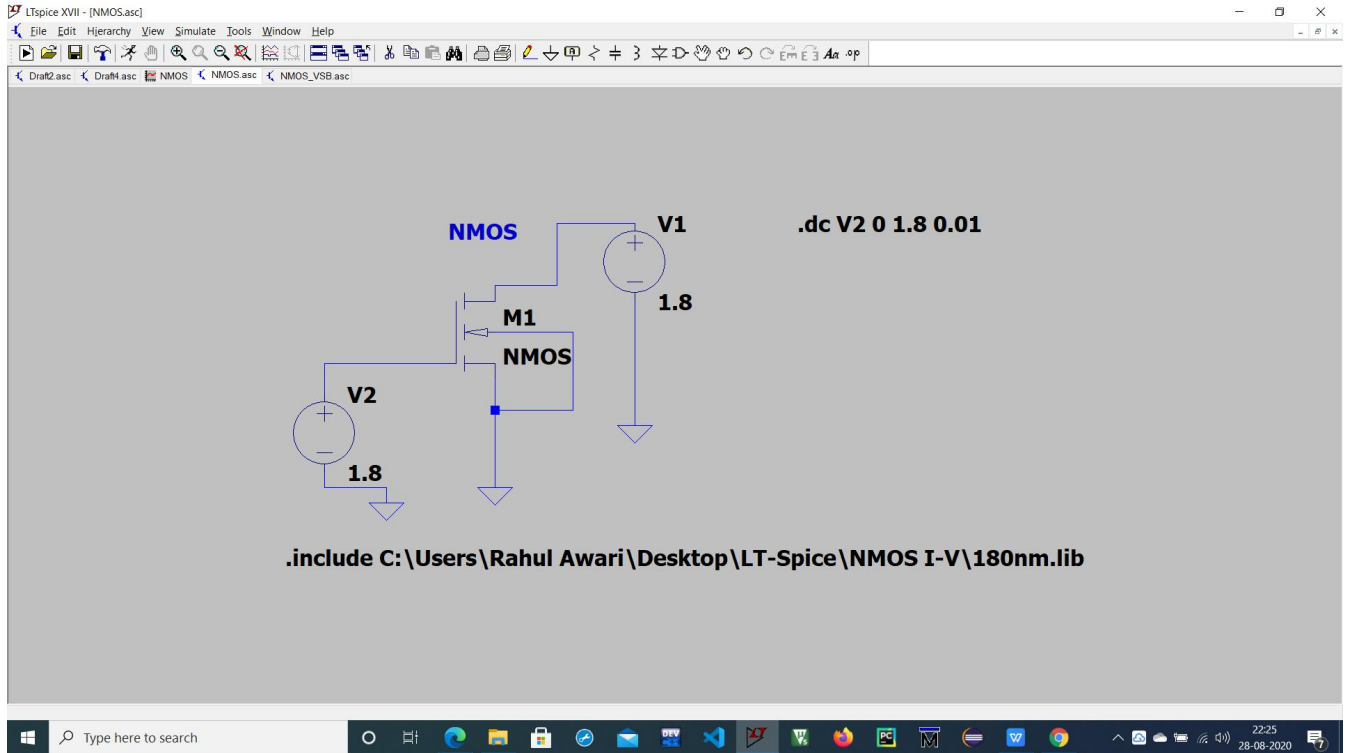
### 3) For calculating $I_{\text{reference}}$ (reference current) for $V_{\text{th0}}$ at 355mV



#### 4) Plot for $I_{ds}$ vs $V_{gs}$ for $V_{sb}(0 \rightarrow 1.8V)$ at interval of 0.6V

Graph:-

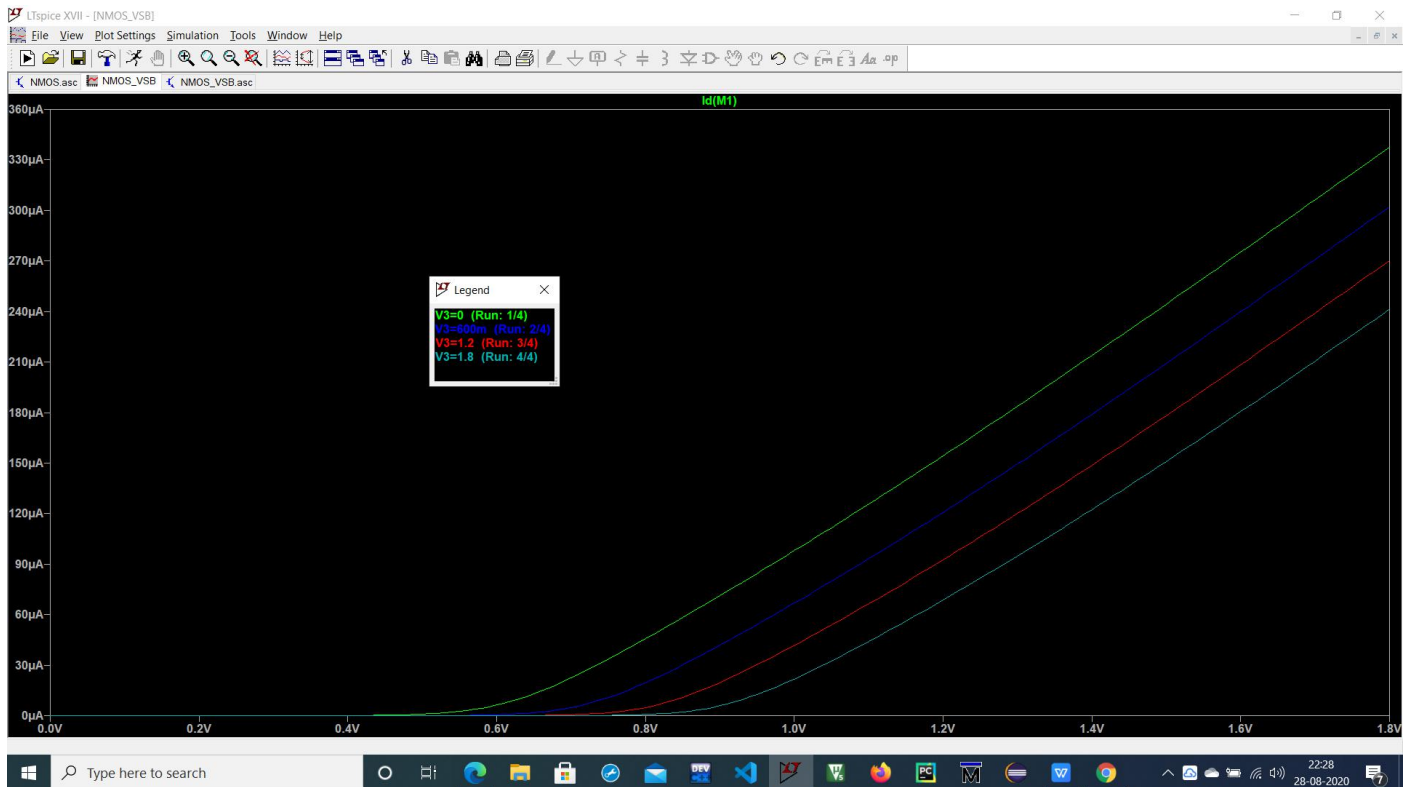

#### CALCULATIONS FOR NMOS:-

$$V_{th0}=355mV$$

$$V_{dsat}=V_{gs}-V_{th0}$$

Table for  $V_{gs}$  and  $V_{dsat}$ :-

$V_{gs}$	$V_{dsat}$
0.6V	0.245V
1.2V	0.845V
1.8V	1.445V

For Channel length modulation Calculation:-

$$V_{ds1}=1.2V$$

$$V_{ds2}=1.6V$$

$$I_{ds2}=151.753\mu A$$

$$I_{ds1}=146.442\mu A$$

$$\lambda = 0.1017$$



$$I_{reference} = 29.830nA$$

**Table:- $V_t$  for  $V_{sb}>0$  by using  $I_{ref}$**


Vsb	Vth
0V	355.700mV
0.6V	484.690mV
1.2V	591.205mV
1.8V	684.039mV

## PMOS


### SCHEMATIC:-

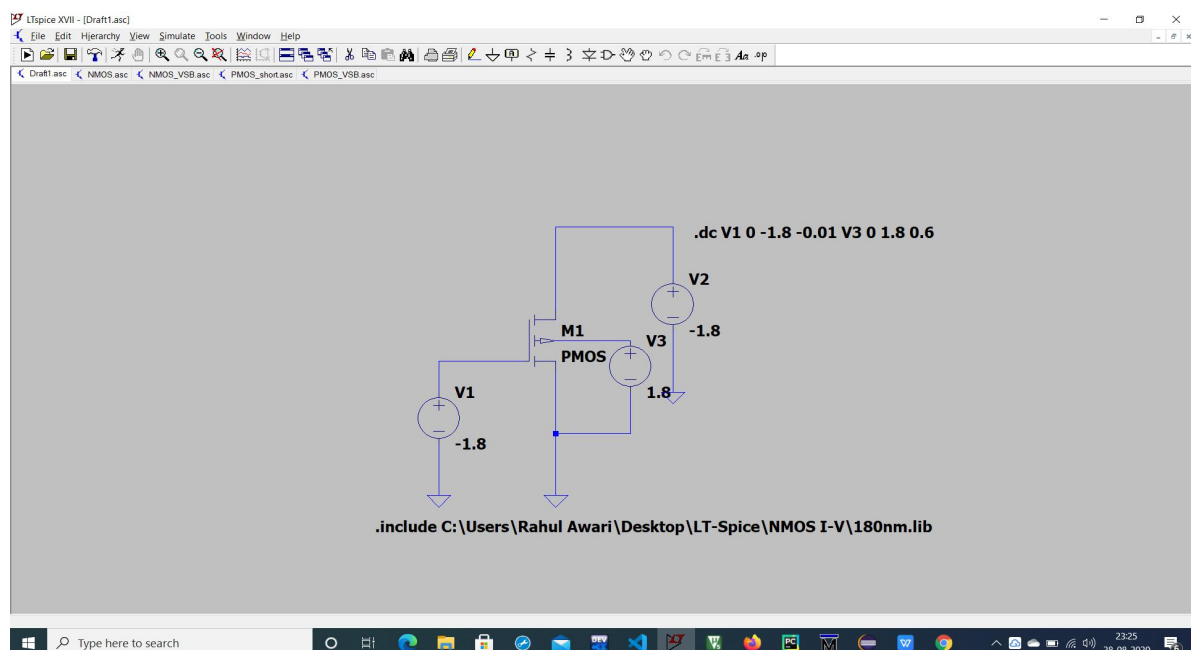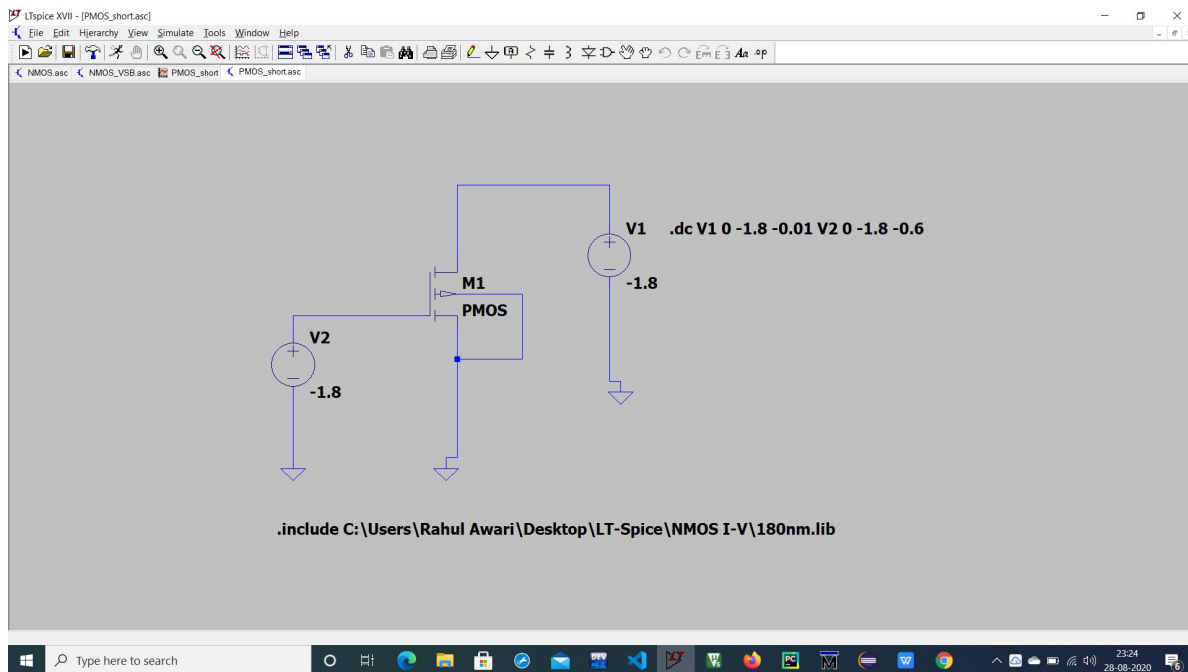



## GRAPHS:- Screen Shot:-

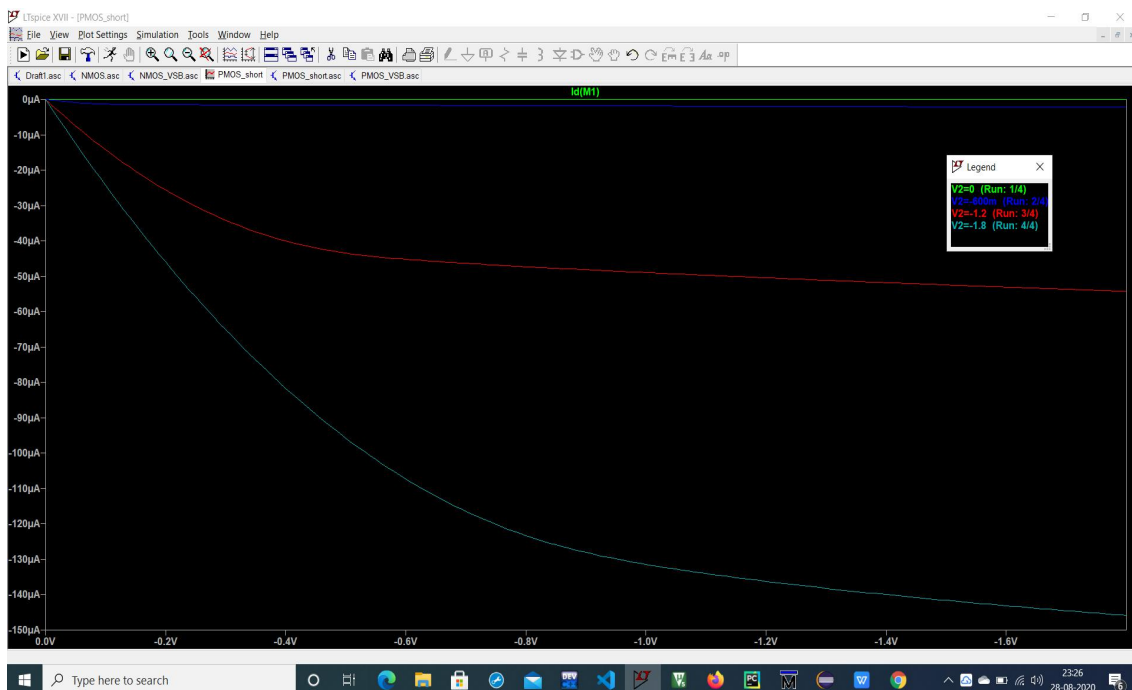

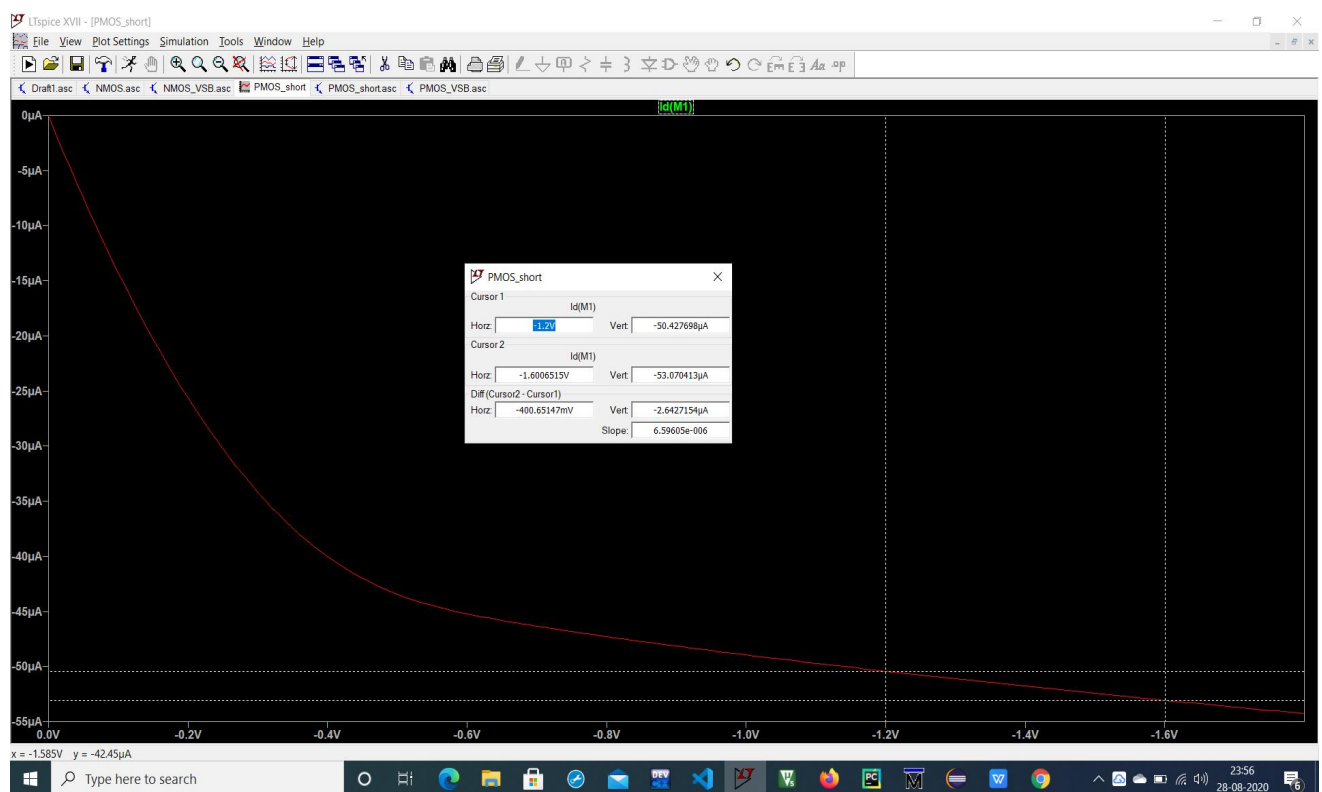2) To Calculate channel Length modulation  $V_{ds1} = -1.2V$  and  $V_{ds2} = -1.6V$  for  $V_{gs} = 1.2V$



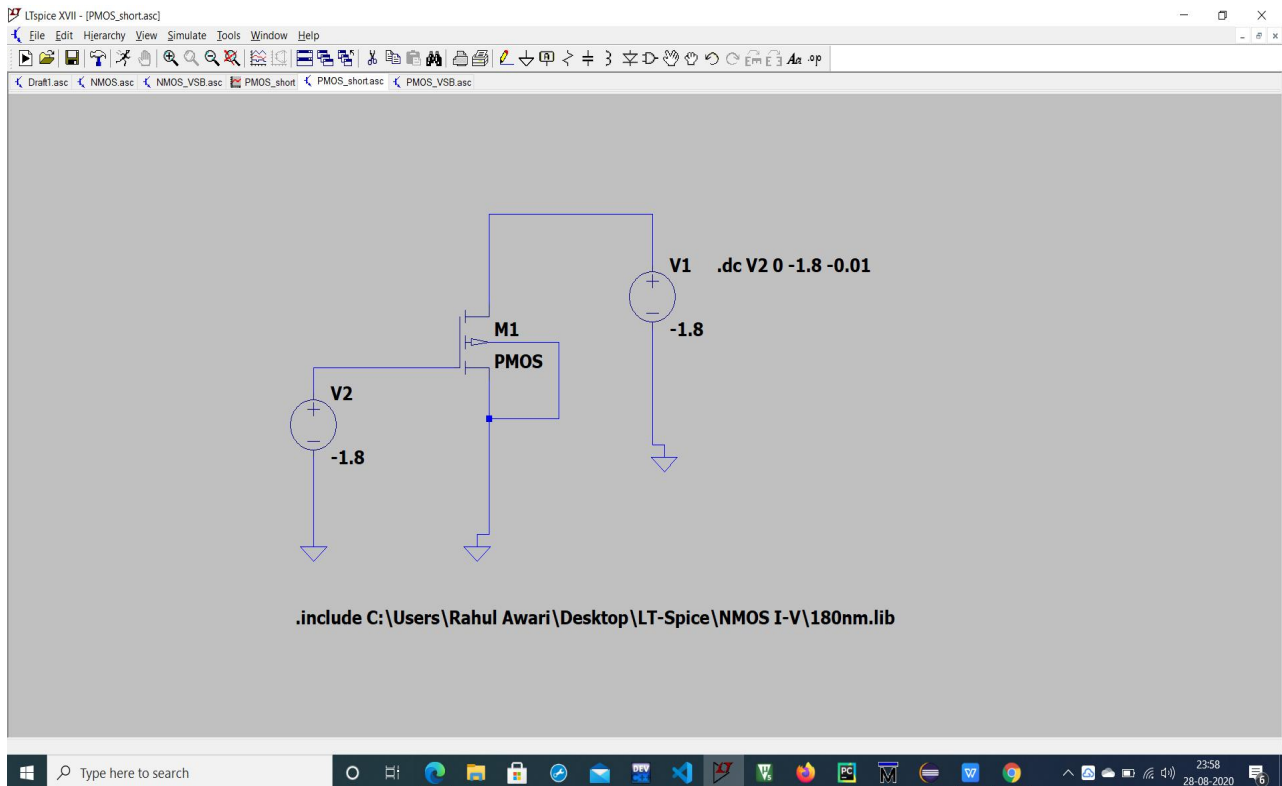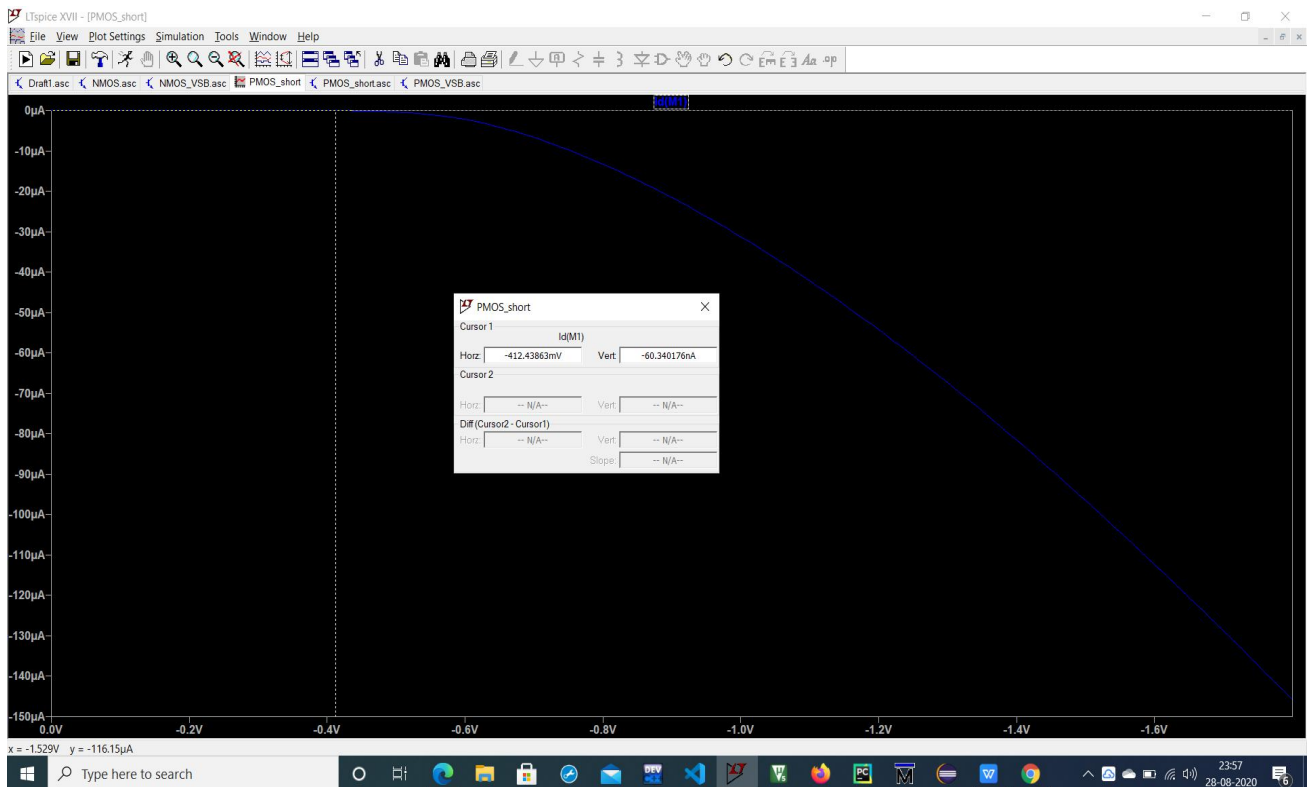
### 3) To plot $I_{ref}$ (reference current) with $v_{tp} = -412.43\text{mV}$




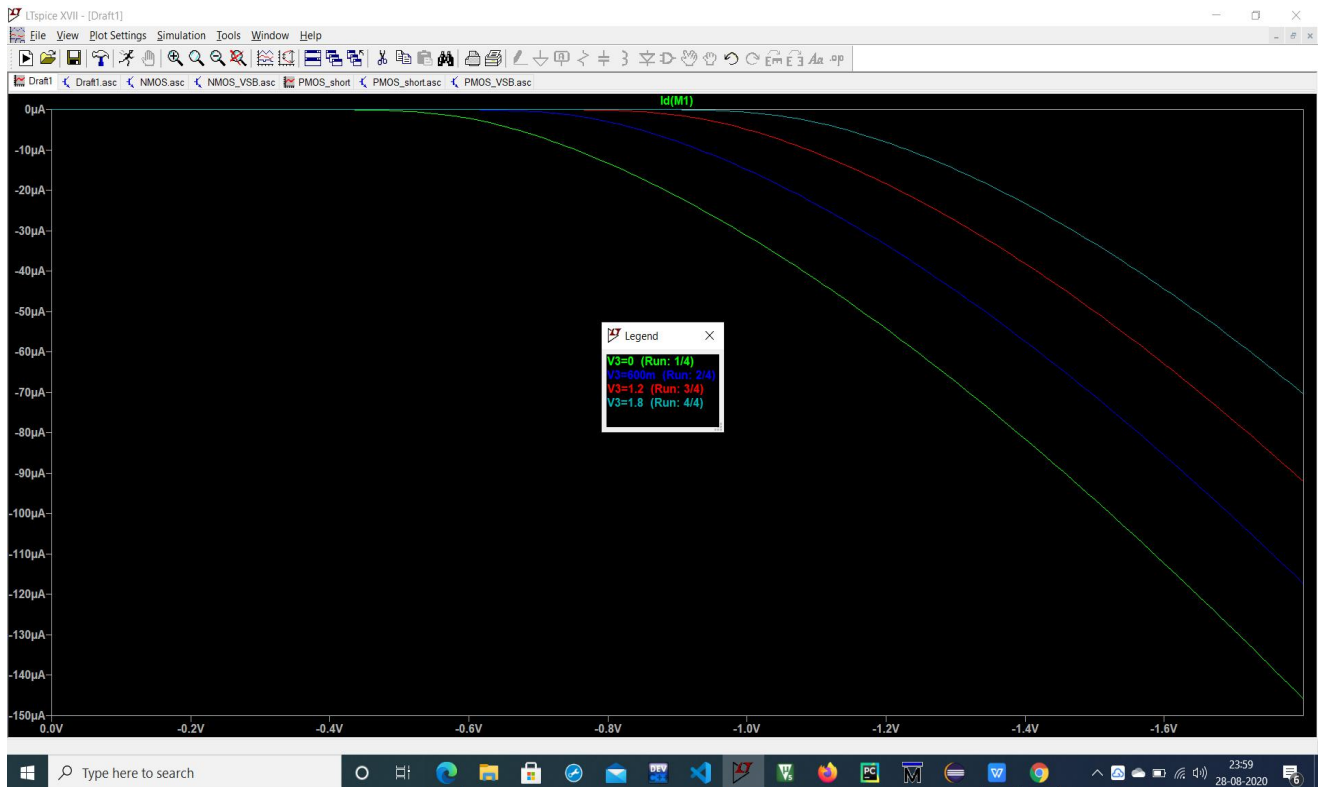
#### 4) To Plot $I_{ds}$ Vs $V_{gs}$ for $V_{sb}(0 \rightarrow -1.8V)$ at interval of $-0.6V$



#### Calculations for PMOS:-

$V_{tp} = -0.412V$

Table for  $V_{gs}$  and  $V_{dsat}$ :-

$V_{gs}$	$V_{dsat}$
-0.6V	-0.188V
-1.2V	-0.788V
-1.8V	-1.388V

For Calculation of Channel length modulation:-

$V_{ds1} = -1.2V$

$V_{ds2} = -1.6V$

$I_{ds1} = -50.427\mu A$

$I_{ds2} = -53.070\mu A$

$\lambda = 0.1562$

$I_{reference} = -60.34nA$

**Table of  $V_t$  for different  $V_{sb}$ :-**

$V_{sb}$	$V_t$
0V	-412.43mV
-0.6V	-594.10mV
-1.2V	-750.48mV
-1.8V	-891.20mV

**Inference for Both PMOS and NMOS:-**

- 1) Length:-180n and Width=500n is for both NMOS and PMOS.
- 2)  $V_{thn}$  and  $V_{thp}$  is observed for both NMOS and PMOS which is required for plotting and calculation of  $I$  reference.
- 3)  $V_{dsat} = V_{gs} - V_{thn}$  is calculated for observing cutoff, saturation and linear region in  $I_d$  Vs  $V_{ds}$  graph. For NMOS with  $V_{gs}=1.2V$ ,  $V_{ds}=1.2V, 1.6V$  were taken for calculation and similarly for PMOS.
- 4)  $V_{dsat}$  is observed for PMOS and NMOS and for calculation of channel length modulation  $V_{ds1}$  and  $V_{ds2}$  is taken from both saturation region of graph of  $I_d$  vs  $V_{ds}$ .
- 5)  $V_{ds1}, V_{ds2}, I_{d1}, I_{d2}$  are used to calculate channel length modulation.
- 6) The  $I$  reference obtained at  $V_{thn}$  and  $V_{thp}$ , is used to obtain  $V_t$  for different Voltage and curve of  $V_{sb}$  where initially source to body voltage is observed to be 0V.
- 7) The body effect of NMOS i.e. plot of  $I_{ds}$  vs  $V_{gs}$  as over different value of  $V_{sb}$  is plotted and the value of threshold voltage for different  $V_{sb}$  values are tabulated. The voltage difference between the source and the bulk,  $V_{sb}$  changes the width of the depletion layer and therefore also the voltage across the oxide due to the change of the charge in the depletion region
- 8) The transfer characteristic is the drain current ( $I_{ds}$ ) response to the input gate-source voltage ( $V_{gs}$ ). Since the gate terminal is electrically isolated from the remaining terminals the gate current is zero, so that gate current is not part of device characteristics.